

LAB 03

MELİKE

DEMİRCİ

21702346

12/03/2020

b) Behavioral SystemVerilog module for 3-to-8 decoder and a testbench for it


```
module decoder3to8 ( input logic in2, in1, in0,  
                    output logic y7, y6, y5, y4, y3, y2, y1, y0) ;  
  
    assign y7 = in2 & in1 & in0 ;  
    assign y6 = in2 & in1 & ~in0  
    assign y5 = in2 & ~in1 & in0  
    assign y4 = in2 & ~in1 & ~in0  
    assign y3 = ~in2 & in1 & in0  
    assign y2 = ~in2 & in1 & ~in0  
    assign y1 = ~in2 & ~in1 & in0  
    assign y0 = ~in2 & ~in1 & ~in0  
  
endmodule
```

```
module decoder3to8_tb();  
  
    logic in2, in1, in0;  
  
    logic y7, y6, y5, y4, y3, y2, y1, y0;  
  
    decoder3to8 decoder(in2, in1, in0, y7, y6, y5, y4, y3, y2, y1, y0); // instantiate dut  
  
    initial begin  
        in2 = 0; in1 = 0; in0 = 0; #100;  
        in2 = 1; in1 = 0; in0 = 0; #100;  
        in2 = 0; in1 = 1; in0 = 0; #100;  
        in2 = 1; in1 = 1; in0 = 0; #100;  
        in2 = 0; in1 = 0; in0 = 1; #100;  
        in2 = 1; in1 = 0; in0 = 1; #100;  
        in2 = 0; in1 = 1; in0 = 1; #100;  
        in2 = 1; in1 = 1; in0 = 1; #100;  
    end  
  
endmodule
```

c) Behavioral SystemVerilog module for 4-to-1 multiplexer.

```
module mux4to1( input logic in3, in2, in1, in0, s1, s0,  
               output logic y);  
    assign out = s1 ? (s0 ? in3 : in2) : (s0 ? in1 : in0);  
endmodule
```

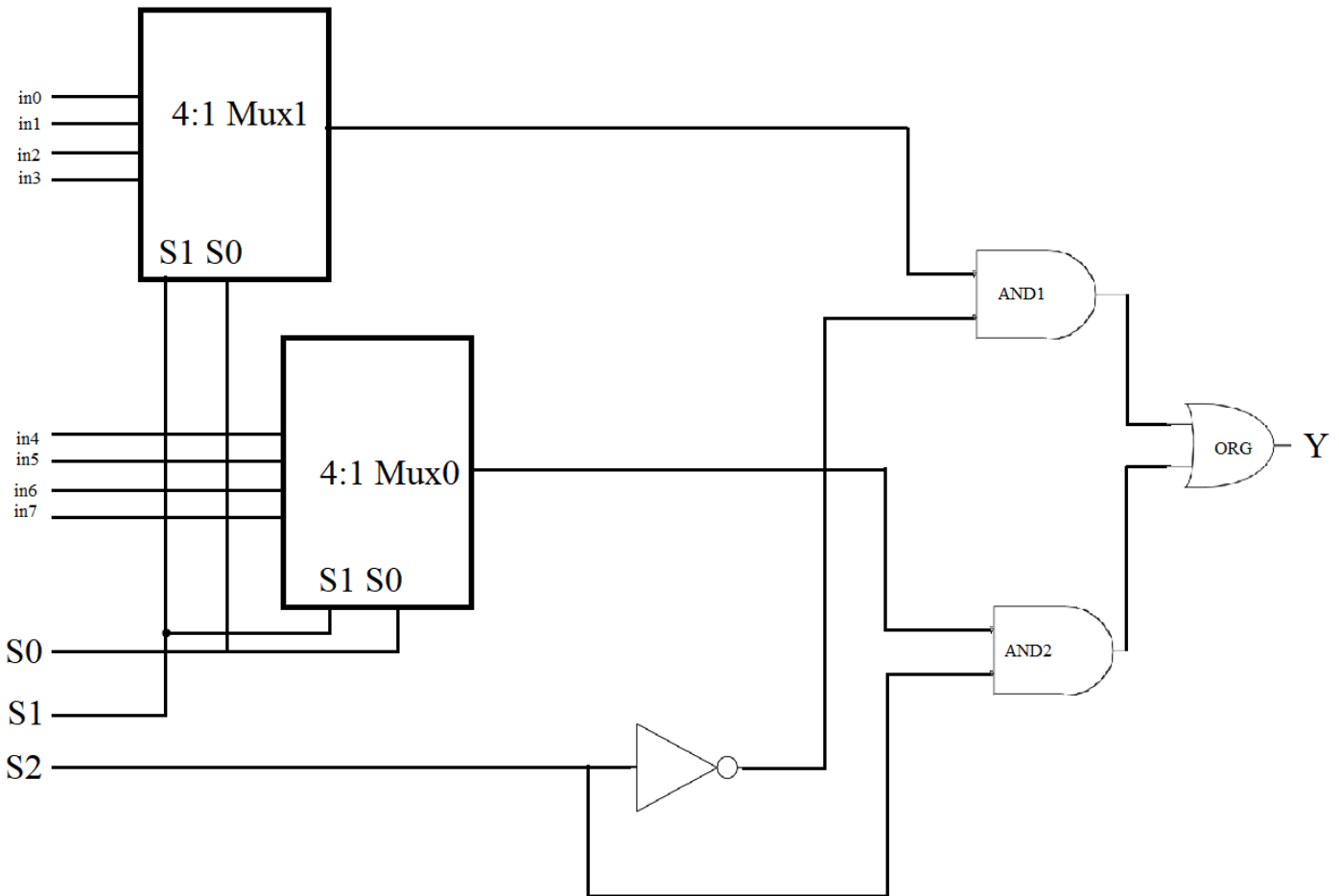(d) Circuit Schematic of 8:1 Multiplexer(two 4:1 multiplexers, an INVERTER, two AND, an OR)




(e) Structural SystemVerilog module for the 8:1 multiplexer and test bench

```
module mux8to1( input logic in0, in1, in2, in3, in4, in5, in6, in7, s2, s1, s0,
                output logic y);
    logic y1, y2, c, e, d;
    mux4to1 mux1(in3, in2, in1, in0, s1, s0, y1);
    mux4to1 mux2(in7, in6, in5, in4, s1, s0, y2);
    not notgate(c, s2);
    and and1(d, y1, c);
    and and2(e, y2, s2);
    or org(y, e, d);
endmodule
```

```
module mux8to1_tb();
    logic in0, in1, in2, in3, in4, in5, in6, in7, s0, s1, s2;
    logic y;
    mux8to1 mux(in0, in1, in2, in3, in4, in5, in6, in7, s0, s1, s2, y); // instantiate dut
    initial begin // apply inputs, check results one at a time
        in0 = 1; in1 = 0; in2 = 1; in3 = 0; in4 = 0; in5 = 1; in6 = 1; in7 = 1; s0 = 0; s1 = 0; s2 = 0; #100;
        s0 = 0; s1 = 0; s2 = 1; #100;
        s0 = 0; s1 = 1; s2 = 0; #100;
        s0 = 0; s1 = 1; s2 = 1; #100;
        s0 = 1; s1 = 0; s2 = 0; #100;
        s0 = 1; s1 = 0; s2 = 1; #100;
        s0 = 1; s1 = 1; s2 = 0; #100;
        s0 = 1; s1 = 1; s2 = 1; #100;
    end
endmodule
```

(f) Circuit schematic for function $F(A,B,C,D) = \sum(1, 2, 7, 8, 9, 10, 12, 13)$

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

 

(g) Structural SystemVerilog module for function and testbench

```

module function(input logic A, B, C, D,
                output Y);

    logic c;

    not notgate(c, C);

    mux8to1 mux(C,c,A,C,A,c,c,c, A, B, D, y);

endmodule

```

```

module function_tb();

```

```

    logic A, B, C, D;

```

```

    logic Y;

```

```

    function f(A, B, C, D, Y); // instantiate dut

```

```

        initial begin

```

```

            A = 0; B = 0; C = 0; D = 0; #100;

```

```

            A = 0; B = 0; C = 0; D = 1; #100;

```

A = 0; B = 0; C = 1; D = 0; #100;

A = 0; B = 0; C = 1; D = 1; #100;

A = 0; B = 1; C = 0; D = 0; #100;

A = 0; B = 1; C = 0; D = 1; #100;

A = 0; B = 1; C = 1; D = 0; #100;

A = 0; B = 1; C = 1; D = 1; #100;

A = 1; B = 0; C = 0; D = 0; #100;

A = 1; B = 0; C = 0; D = 1; #100;

A = 1; B = 0; C = 1; D = 0; #100;

A = 1; B = 0; C = 1; D = 1; #100;

A = 1; B = 1; C = 0; D = 0; #100;

A = 1; B = 1; C = 0; D = 1; #100;

A = 1; B = 1; C = 1; D = 0; #100;

A = 1; B = 1; C = 1; D = 1; #100;

end

endmodule