

# **CS 223 - Digital Design**

Melike Demirci

21702346

Section 4

Lab02

02/03/2020

b) Circuit schematic for full adder using 2-input XOR, AND and OR gates

 


Figure 1 – Full Adder Circuit Schematic

$$S = (A \oplus B) \oplus \text{Cin}$$

$$\text{Cout} = AB + \text{Cin}(A \oplus B)$$

(c) Circuit schematic for full subtractor

 


Figure 2 – Full Subtractor Circuit Schematic

$$D = (A \oplus B) \oplus \text{Bin}$$

$$\text{Bout} = \sim AB + \text{Bin} \sim (A \oplus B)$$

(d) Circuit schematic for a 2-bit adder made from two full adders

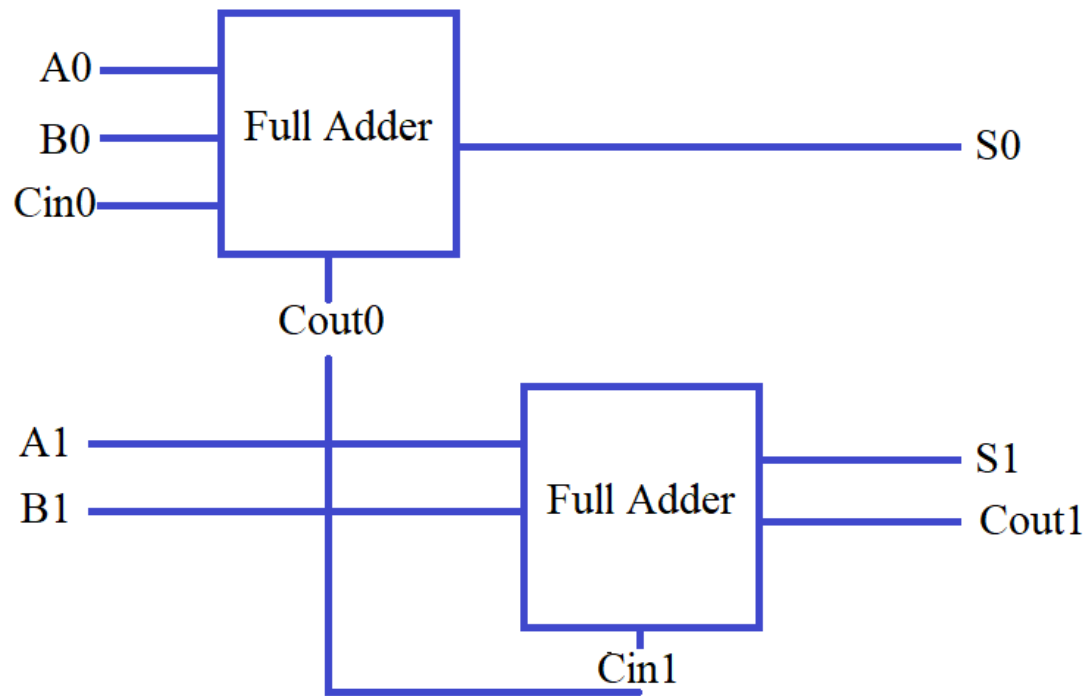


Figure 3 – 2-bit Adder Circuit Schematic

(e) Behavioral System Verilog module for the full adder and a testbench for it.

**//Behavioral System Verilog module for a 1-bit Full Adder**

```
module one_bit_full_adder_behavioral (input logic a, b, cin, output logic s, cout);  
    assign s = a ^ b ^ cin;  
    assign cout = a & b | (a ^ b) & cin;  
endmodule
```

**//Testbench**

```
module one_bit_full_adder_behavioral_tb();  
    logic a, b, cin, s, cout;  
    one_bit_full_adder_behavioral fab(a, b, cin, s, cout);  
    initial begin  
        a = 0; b = 0; cin = 0;      #10  
        cin = 1;                    #10  
        b = 1; cin = 0;              #10  
        cin = 1;                    #10  
        a = 1; b = 0; cin = 0;      #10  
        cin = 1;                    #10  
        b = 1; cin = 0;              #10  
        cin = 1;                    #10  
    end  
endmodule
```

(f) Structural System Verilog module for the full adder and a testbench for it.

**//Structural System Verilog module for a 1-bit Full Adder**

```
module one_bit_full_adder_structural (a, b, cin, s, cout);
```

```
    logic n1, n2, n3;
```

```
    xor xor_1(n1, a, b);
```

```
    xor xor_2(s, n1, cin);
```

```
    and and_1(n2, a, b);
```

```
    and and_2(n3, n1, n2);
```

```
    or or_1(cout, n3, n2);
```

```
end module
```

**//Testbench**

```
module one_bit_full_adder_structural_tb();
```

```
    logic a, b, cin, s, cout;
```

```
    one_bit_full_adder_structural fas(a, b, cin, s, cout);
```

```
    initial begin
```

```
        a = 0; b = 0; cin = 0;          #10
```

```
        cin = 1;                        #10
```

```
        b = 1; cin = 0;                 #10
```

```
        cin = 1;                        #10
```

```
        a = 1; b = 0; cin = 0;         #10
```

```
        cin = 1;                        #10
```

```
        b = 1; cin = 0;                 #10
```

```
        cin = 1;                        #10
```

```
    end
```

```
endmodule
```

(g) Structural System Verilog module for the full subtractor and a testbench for it.

**//Structural System Verilog module for a 1-bit Full Subtractor**

```
module one_bit_full_subtractor_structural (a, b, bin, d, bout);  
    logic n1, n2, n3;  
    xor xor_1 (n1, a, b);  
    xor xor_2(d, n1, bin);  
    and and_1 (n2, ~a, b);  
    and and_2(n3, ~n1, bin);  
    or or_1 (bout, n3, n2);
```

```
end module
```

**//Testbench**

```
module one_bit_full_subtractor_structural_tb();  
    logic a, b, bin, d, bout;  
    one_bit_full_subtractor_structural fss(a, b, bin, d, bout);  
  
    initial begin  
        a = 0; b = 0; bin = 0;      #10  
        bin = 1;                    #10  
        b = 1; bin = 0;             #10  
        bin = 1;                    #10  
        a = 1; b = 0; bin = 0;      #10  
        bin = 1;                    #10  
        b = 1; bin = 0;             #10  
        bin = 1;                    #10  
    end  
endmodule
```

(h) Structural System Verilog module for the 2-bit adder and a testbench for it.

**//Structural System Verilog module for a 2-bit adder**

```
module two_bit_adder (input logic a0, a1, b0, b1, cin0, output logic s0, s1, cout1);  
  
    logic cout;  
  
    one_bit_full_adder_structural full_adder(a0, b0, cin0, s0, cout);  
  
    one_bit_full_adder_structural full_adder2(a1, b1, cout, s1, cout1)  
  
endmodule
```

**//Testbench**

```
module two_bit_adder_tb();  
  
    logic a0, a1, b0, b1, cin0;  
  
    logic s0, s1, cout1;  
  
    two_bit_adder tba(a0, a1, b0, b1, cin0, s0, s1, cout1);  
  
    initial begin  
  
        a0= 0; a1=0; b0=0; b1=0; cin0=0; #10; //00000 failed  
  
        a0= 0; a1=0; b0=0; b1=0; cin0=1; #10; //00001 failed  
  
        a0= 0; a1=0; b0=0; b1=1; cin0=0; #10; //00010 failed  
  
        a0= 0; a1=0; b0=0; b1=1; cin0=1; #10; //00011 failed  
  
        a0= 0; a1=0; b0=1; b1=0; cin0=0; #10; //00100 failed  
  
        a0= 0; a1=0; b0=1; b1=0; cin0=1; #10; //00101 failed  
  
        a0= 0; a1=0; b0=1; b1=1; cin0=0; #10; //00110 failed  
  
        a0= 0; a1=0; b0=1; b1=1; cin0=1; #10; //00111 failed  
  
        a0= 0; a1=1; b0=0; b1=0; cin0=0; #10; //01000 failed  
  
        a0= 0; a1=1; b0=0; b1=0; cin0=1; #10; //01001 failed  
  
        a0= 0; a1=1; b0=0; b1=1; cin0=0; #10; //01010 failed  
  
        a0= 0; a1=1; b0=0; b1=1; cin0=1; #10; //01011 failed  
  
        a0= 0; a1=1; b0=1; b1=0; cin0=0; #10; //01100 failed  
  
        a0= 0; a1=1; b0=1; b1=0; cin0=1; #10; //01101 failed
```

```

a0= 0; a1=1; b0=1; b1=1; cin0=0; #10; //01110 failed
a0= 0; a1=1; b0=1; b1=1; cin0=1; #10; //01111 failed
a0= 1; a1=0; b0=0; b1=0; cin0=0; #10; //10000 failed
a0= 1; a1=0; b0=0; b1=0; cin0=1; #10; //10001 failed
a0= 1; a1=0; b0=0; b1=1; cin0=0; #10; //10010 failed
a0= 1; a1=0; b0=0; b1=1; cin0=1; #10; //10011 failed
a0= 1; a1=0; b0=1; b1=0; cin0=0; #10; //10100 failed
a0= 1; a1=0; b0=1; b1=0; cin0=1; #10; //10101 failed
a0= 1; a1=0; b0=1; b1=1; cin0=0; #10; //10110 failed
a0= 1; a1=0; b0=1; b1=1; cin0=1; #10; //10111 failed
a0= 1; a1=1; b0=0; b1=0; cin0=0; #10; //11000 failed
a0= 1; a1=1; b0=0; b1=0; cin0=1; #10; //11001 failed
a0= 1; a1=1; b0=0; b1=1; cin0=0; #10; //11010 failed
a0= 1; a1=1; b0=0; b1=1; cin0=1; #10; //11011 failed
a0= 1; a1=1; b0=1; b1=0; cin0=0; #10; //11100 failed
a0= 1; a1=1; b0=1; b1=0; cin0=1; #10; //11101 failed
a0= 1; a1=1; b0=1; b1=1; cin0=0; #10; //11110 failed
a0= 1; a1=1; b0=1; b1=1; cin0=1; #10; //11111 failed

```

```

end

```

```

endmodule

```